

Drawing Circuits

Draw the following circuits using a ruler and a pencil.

Remember to use the correct symbols, and circuits always have straight lines!

1. Draw a circuit with a **cell**, **globe** and **switch**.

2. Draw a circuit with a **battery**, **3 globes in series** and a **switch**.

3. Draw a circuit with a **battery** and **3 globes in parallel**.

4. Draw a circuit with a **cell**, **3 globes in parallel** and a **switch** on the **second globe**.

Name	Symbol	Name	Symbol
electrochemical cell		conductor wire	
battery		light globe	
open switch		resistor	
closed switch		variable resistor	
ammeter		voltmeter	

5. Draw a circuit with a **battery**, **2 globes**, a **switch** and an **ammeter**.

6. Draw a circuit with a **cell**, **2 globes in series** and a **voltmeter** on the **second globe**.

7. Draw a circuit with a **battery**, **resistor**, **switch** and **globe in series**.

8. Draw a circuit with a **variable resistor**, **switch**, **globe** and **ammeter**